



- LeBlanc transformer is a 3 phase transformer.
- The terminals A,B and C are connected to the symmetrical 3 phase net:  $U_A = U_B = U_C = U$
- The output power of the load is equal:  $S = U_L I_L = P + jQ$ ,  $\text{tg}(\varphi) = Q/P$ . Normally the output voltages  $U_L$  are equal and the load resistive ( $Q = 0$ ,  $\varphi = 0$ ).
- The secondary winding with voltage  $U_a$  is wound on the center leg.
- $U_a = 2 U_L / 3$
- $U_{b1} = U_{c1} = U_L / 1.73$
- $U_{b2} = U_{c2} = U_L / 3$
- $\hat{I}_A = (U_a / U_A) I_L e^{j\varphi}$ ,  $\hat{I}_B = \hat{I}_A e^{j2\pi/3}$ ,  $\hat{I}_C = \hat{I}_A e^{-j2\pi/3}$
- 
- **Creating the inputs in the Large Transformers Program for  $\varphi = 0$**
- 

**Design 1 on the leg A:**

- Primary voltage =  $U$
- Secondary voltage =  $U_a$
- Secondary current =  $I_L$ , Angle =  $0^\circ$  degrees

**Design 2 on the leg IB or C:**

- Primary voltage =  $U$
- Secondary voltage 1 =  $U_L / 1.73$
- Secondary current 1 =  $I_L$ , Angle =  $+60^\circ$

- Secondary voltage 2 =  $U_L / 3$
- Secondary current 2 =  $I_L$ , Angle =  $300^\circ$

- The results of the Design 1 need to be wound on the leg A. The results of the Design 2 need to be wound on the Leg B and C. The primary windings on the legs A,B and C has to be equal.